



Circuits

Record observations from your experiment.

Color in the light bulb that would turn on in the two circuits below. One is a closed circuit, and one is an open circuit. Can you label them?


