



Circuits

Write any notes about circuits from your assignments today.

Explain an open circuit.
Draw an example.

Explain a closed circuit.
Draw an example.

